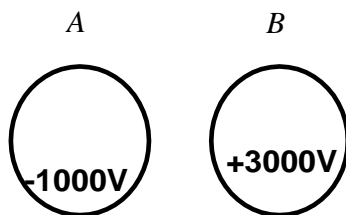




**WORKSHEET**  
**CHAPTER 12 - ELECTRICITY**


**CLASS: X (CBSE)****SUBJECT: PHYSICS****NUMERICAL PROBLEMS**

1. Find the charge if the number of electrons is  $4 \times 10^{-18}$ .
2. Find the number of electrons constituting one coulomb of charge.
3. How much work done in moving a charge of 3 coulombs from a point at 118 V to a point at 128volt?
4. How much work done in moving a charge of 2C across two points having a potential difference of 12V?
5. Calculate the amount of work done to carry 4C from a point at 100 V to a point at 120volt?
6. How much work will be done in bringing a charge of  $2 \times 10^{-3}$  coulombs from infinity to a point P at which the potential is 5V?
7. How much work will be done in bringing a charge of  $3 \times 10^{-2}$  coulombs from infinity to a point P at which the potential is 20V?
8. How much energy is given to each coulomb of charge passing through a 6V battery?
9. How much energy is transferred by a 12 V power supply to each coulomb of charge which it moves around a circuit?
10. What is the potential difference between the terminals of a battery if 250 joules of work is required to transfer 20 coulombs of charge from one terminal of battery to the other?
11. What is the potential difference between the conductors A and B shown in below figure? If the conductors are connected by a length of wire, which way will electrons flow? When will this flow of electrons stop?



12. A particle of charge 2C is taken from a point at a potential of 100V to another point at a potential of 150V. Calculate the work done.

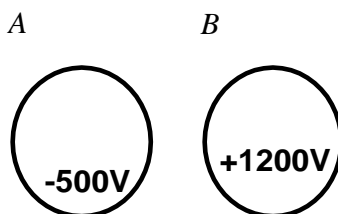13. What is the potential difference between the conductors A and B shown in below figure? If the conductors are connected by a length of wire, which way will electrons flow? When will this flow of electrons stop?



14. A particle of charge  $5 \times 10^{-2} \text{ C}$  is taken from a point at a potential of 50V to another point at a potential of 250V. Calculate the workdone.
15. Three 2V cells are connected in series and used as a battery in a circuit.
- (a) What is the potential difference at the terminals of the battery?
- (b) How many joules of electrical energy does 1 C gain on passing through (i) one cell (ii) all three cells.

### NUMERICAL PROBLEMS

1. What current must flow if 0.24 coulombs is to be transferred in 15ms?
2. If a current of 10 A flows for four minutes, find the quantity of electricity transferred.
3. An electric bulb draws a current of 0.25A for 20 minutes. Calculate the electric charge that flows through the circuit.
4. If the amount of electric charge passing through a conductor in 10min is 300C, find the current.
5. How many electrons are flowing per second past a point in a circuit in which there is a current of 4A?
6. A lamp of resistance  $80\Omega$  draw a current of 0.75A. Find the line voltage.
7. A electric heater draw a current of 5A when connected to 220V mains. Calculate the resistance of its filament.
8. How much current will an electric bulb draw from a 200V source, if the resistance of the filament is  $1200\Omega$ ?
9. How much current will an electric heater draw from a 200V source, if the resistance of the filament is  $100\Omega$ ?
10. How much current does an electric heater draw from a 220V line, if the resistance of the heater (when hot) is  $50\Omega$ ?
11. A bulb when cold has  $1\Omega$  resistance. It draws a current of 0.3A when glowing from a source of 3V. Calculate the resistance of the bulb when flowing and explain the reason for the difference in resistance.

12. Calculate the potential difference required across a conductor of resistance  $5\Omega$  to make a current of  $1.5\text{A}$  flow through it.
13. What is the resistance of an electric lamp when hot, if the lamp uses  $20\text{A}$  when connected to a  $220\text{V}$  line?
14. Calculate the amount of work done to draw a current of  $8\text{A}$  from a point at  $100\text{V}$  to a point at  $120\text{V}$  in  $2$  seconds.
15. If  $200\text{C}$  of charge pass a point in a circuit in  $4$  sec, what current is flowing?
16. A current of  $4\text{A}$  flows around a circuit in  $10$  seconds. How much charge flows past a point in the circuit in this time? Also find the number of electrons that pass in the circuit.
17. The current flowing through a resistor is  $0.8\text{ A}$  when a p.d. of  $20\text{ V}$  is applied. Determine the value of the resistance.
18. Determine the p.d. which must be applied to a  $2\text{ k}\Omega$  resistor in order that a current of  $10\text{ mA}$  may flow.
19. A coil has a current of  $50\text{ mA}$  flowing through it when the applied voltage is  $12\text{ V}$ . What is the resistance of the coil?
20. A  $100\text{ V}$  battery is connected across a resistor and causes a current of  $5\text{ mA}$  to flow. Determine the resistance of the resistor. If the voltage is now reduced to  $25\text{ V}$ , what will be the new value of the current flowing?
21. What is the resistance of a coil which draws a current of (a)  $50\text{ mA}$  and (b)  $200\mu\text{A}$  from a  $120\text{ V}$  supply?
22. If a current of  $5\text{ A}$  flows for  $2$  minutes, find the quantity of electricity transferred.
23. A current of  $0.5\text{ A}$  is drawn by a filament of an electric bulb for  $10$  minutes. Find the amount of electric charge that flows through the circuit.
24. How much current will an electric bulb draw from a  $220\text{ V}$  source, if the resistance of the bulb filament is  $1200\Omega$ ?
25. How much current will an electric heater coil draw from a  $220\text{ V}$  source, if the resistance of the heater coil is  $100\Omega$ ?
26. The potential difference between the terminals of an electric heater is  $60\text{ V}$  when it draws a current of  $4\text{ A}$  from the source. What current will the heater draw if the potential difference is increased to  $120\text{V}$ ?
27. When a  $12\text{ V}$  battery is connected across an unknown resistor, there is a current of  $2.5\text{ mA}$  in the circuit. Find the value of the resistance of the resistor.
28. An electric heater is connected to the  $230\text{ V}$  mains supply. A current of  $8\text{A}$  flows through the heater (a) How much charge flows around the circuit each second. (b) How much energy is transferred to the heater each second?
29. How many electrons are flowing per second past a point in a circuit in which there is a current of  $5\text{A}$ ?

30. An electric iron draws a current of 3.4A from the 220V supply line. What current will this electric iron draw when connected to 110V supply line?
31. A simple electric circuit has a 24V battery and a resistor of  $60\Omega$ . What will be the current in the circuit?
32. When a  $4\Omega$  resistor is connected across the terminal of 12V battery, find the number of coulombs passing through the resistor per second.
33. An electric room heater draw a current of 2.4A from the 120V supply line. What current will this room heater draw when connected to 240V supply line?
34. A current of 200mA flows through a  $4k\Omega$  resistor. What is the p.d. across the resistor?
35. A p.d. of 10V is needed to make a current of 0.02A flow through a wire. What p.d. is needed to make a current of 250mA flow through the same wire?
36. A TV draws a current of 5 A from the 240V supply line. What current will this TV draw when it is connected to 100V supply line.
37. The potential difference between the terminals of an electric heater is 60V when it draw a current of 4A from the source. What current will the heater draw if the potential difference is increased to 120V?
38. A bulb of resistance  $400\Omega$  is connected to 220V mains. Calculate the magnitude of current.
39. A battery of two cells is used to light a torch bulb of resistance  $5\Omega$ . The cells maintain a potential difference of 3V across the bulb. How much current will flow through the bulb?
40. A steady current of 5A flows through a circuit for 30 minutes. How much charge has circulated through the circuit in this time?


#### NUMERICAL PROBLEMS ON RESISTIVITY

1. Calculate the resistance of a copper wire of length 2m and area of cross section  $10^{-6}m^2$ . Resistivity of copper is  $1.7 \times 10^{-8}\Omega m$
2. A copper wire of length 2m and area of cross section  $1.7 \times 10^{-6}m^2$  has a resistance of  $2 \times 10^{-2}$  ohms. Calculate the resistivity of copper.
3. The amount of charge passing through a cell in 12 seconds is 3C. What is the current supplied by the cell?
4. A 12 V battery of a car is connected across a  $4\Omega$  resistor. Calculate the current passing through the resistor.
5. Resistivity of a given copper wire of length 2m is  $1.7 \times 10^{-8}\Omega m$ . The wire is stretched so that its length becomes 4m. Find new resistivity of the copper wire.


6. Resistance of a given wire of length '  $l$  ' is  $3\ \Omega$  . The wire is stretched uniformly such that its length becomes  $2l$ . Find the new resistance of the stretched wire.
7. Resistance of a given wire of length '  $l$  ' is  $4\ \Omega$  . The wire is stretched uniformly such that its length becomes  $3l$ . Find the new resistance of the stretched wire.
8. A copper wire has a diameter of  $0.5\text{ mm}$  and resistivity of  $1.6 \times 10^{-8}\ \Omega\text{m}$ . What will be the length of this wire to make its resistance  $10\ \Omega$  ? How much does the resistance change if the diameter is doubled?
9. A  $6\ \Omega$  resistance wire is doubled up by folding. Calculate the new resistance of the wire.
10. Calculate the resistance of an aluminium cable of length  $10\text{ km}$  and diameter  $20\text{ mm}$  if the resistivity of aluminum is  $2.7 \times 10^{-8}\ \Omega\text{m}$ .
11. Calculate the area of cross section of a wire if its length is  $1.0\text{ m}$ , its resistance is  $23\ \Omega$  and the resistivity of the material of the wire is  $1.84 \times 10^{-6}\ \Omega\text{m}$ .
12. A piece of wire of resistance  $20\ \Omega$  is drawn out so that its length is increased to twice its original length. Calculate the resistance of the wire in the new situation.
13. Two cylindrical wires of the same material have their lengths in the ratio of  $4 : 9$ . What should be the ratio of their radii so that their resistances are in the ratio of  $4 : 1$ ?
14. Two wires of the same metal, have the same area of cross section but their lengths in the ratio of  $3 : 1$ . What should be the ratio of current flowing through them respectively, when the same potential difference is applied across each of their length?
15. Two wires A and B of length  $30\text{ m}$  and  $10\text{ m}$  have radii  $2\text{ cm}$  and  $1\text{ cm}$  respectively. Compare the resistances of the two wires. Which will have less resistance?
16. Calculate the resistance of  $1\text{ km}$  long copper wire of radius  $1\text{ mm}$ . Resistivity of copper is  $1.7 \times 10^{-8}\ \Omega\text{m}$
17. A  $4\ \Omega$  wire is doubled on it. Calculate the new resistance of the wire.
18. What should be the length of the nichrome wire of resistance  $4.5\ \Omega$  , if the length of a similar wire is  $60\text{ cm}$  and resistance  $2.5\ \Omega$ ?
19. A metal wire of resistivity  $64 \times 10^{-6}\ \Omega\text{ m}$  and length  $198\text{ cm}$  has a resistance of  $7\ \Omega$ . Calculate its radius.
20. Calculate the resistivity of the material of a wire  $1.0\text{ m}$  long,  $0.4\text{ mm}$  in diameter and having a resistance of  $2.0\ \Omega$ .
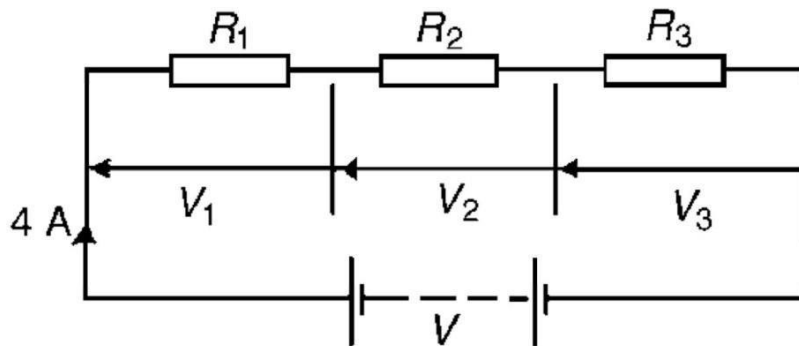
## NUMERICAL PROBLEMS


- For the circuit shown in below Figure, determine (a) the battery voltage  $V$ , (b) the total resistance of the circuit, and (c) the values of resistance of resistors  $R_1$ ,  $R_2$  and  $R_3$ , given that the p.d.'s across  $R_1$ ,  $R_2$  and  $R_3$  are 5 V, 2 V and 6 V respectively.



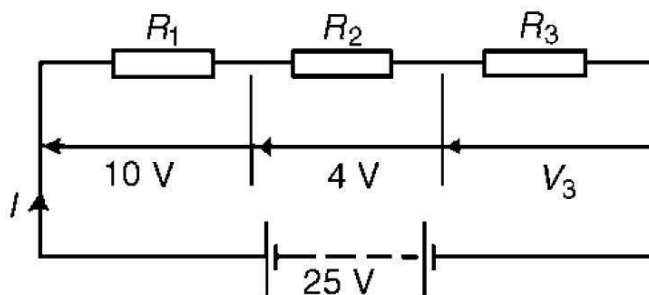
- For the circuit shown in below Figure, determine the p.d. across resistor  $R_3$ . If the total resistance of the circuit is  $100\Omega$ , determine the current flowing through resistor  $R_1$ . Find also the value of resistor  $R_2$ .



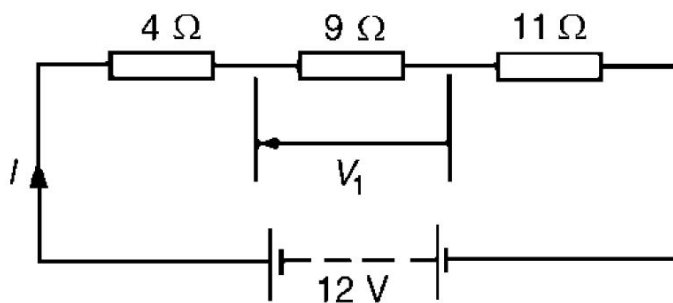
- A  $12\text{ V}$  battery is connected in a circuit having three series-connected resistors having resistances of  $4\Omega$ ,  $9\Omega$  and  $11\Omega$ . Determine the current flowing through, and the p.d. across the  $9\Omega$  resistor.



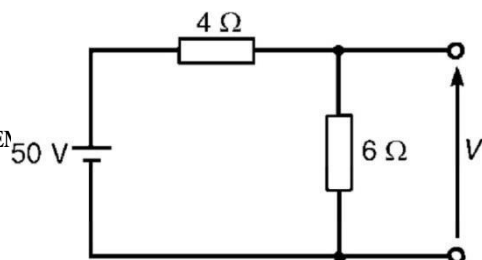
- Find the voltage  $V$  in the given figure.



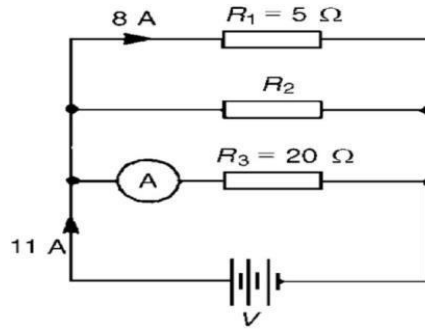
5. For the circuit shown in given Figure, determine (a) the reading on the ammeter, and (b) the value of resistor  $R_2$
6. Two resistors are connected in series across a 24 V supply and a current of 3 A flows in the circuit. If one of the resistors has a resistance of  $2\Omega$  determine (a) the value of the other resistor, and (b) the p.d. across the  $2\Omega$  resistor. If the circuit is connected for 50 hours, how much energy is used?
7. Two resistors, of resistance  $3\Omega$  and  $6\Omega$ , are connected in parallel across a battery having a voltage of 12



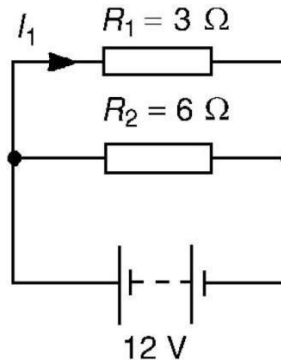
V. Determine (a) the total circuit resistance and (b) the current flowing in the  $3\Omega$  resistor.



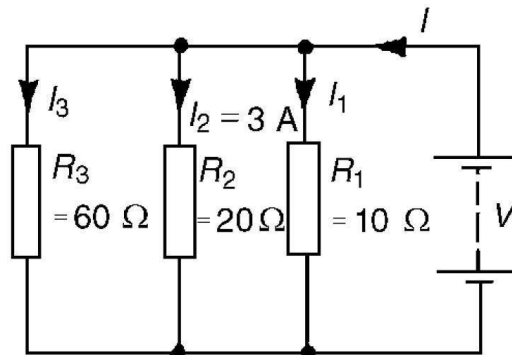
8. For the circuit shown in below Figure, find (a) the value of the supply voltage  $V$  and (b) the value of current  $I$ .



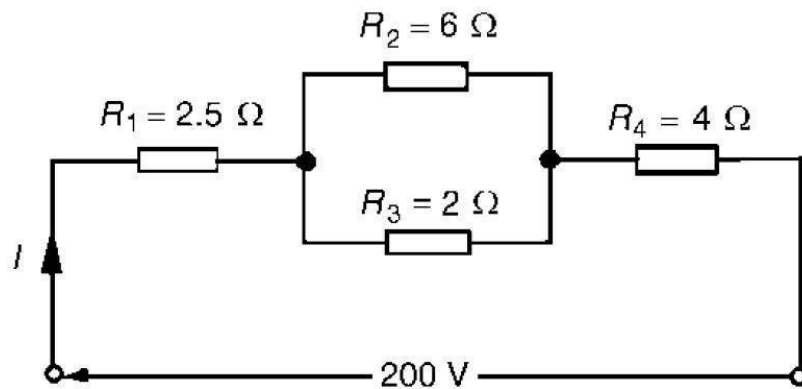
9. For the series-parallel arrangement shown in below Figure, find (a) the supply current, (b) the current flowing through each resistor and (c) the p.d. across each resistor.



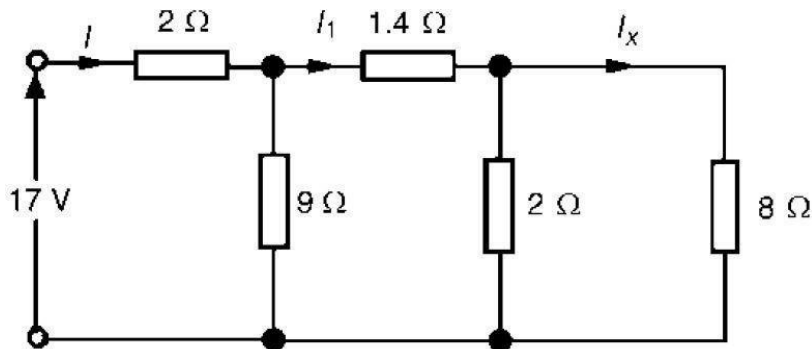10. For the arrangement shown in below Figure, find the current  $I_x$ .




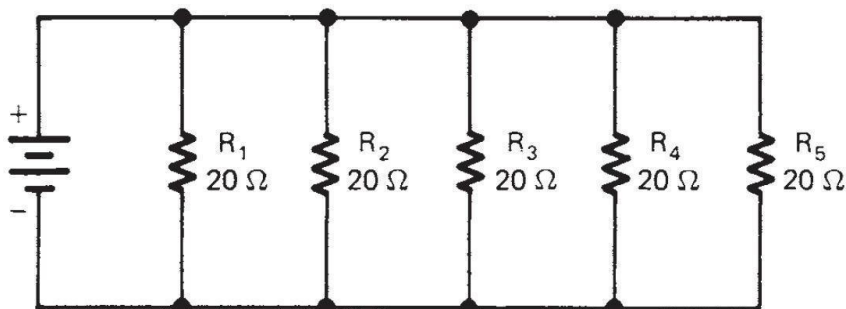11. Four resistances of  $16\ \Omega$  each are connected in parallel. Four such combinations are connected in series. What is the total resistance?
12. A battery of  $9\text{ V}$  is connected in series with resistors of  $0.2\ \Omega, 0.3\ \Omega, 0.4\ \Omega, 0.5\ \Omega$  and  $12\ \Omega$ . How much current would flow through the  $12\ \Omega$  resistor?
13. An electric bulb of resistance  $20\ \Omega$  and a resistance wire of  $4\ \Omega$  are connected in series with a  $6\text{ V}$  battery. Draw the circuit diagram and calculate: (a) total resistance of the circuit (b) current through the circuit (c) potential difference across the electric bulb (d) potential difference across the resistance wire.






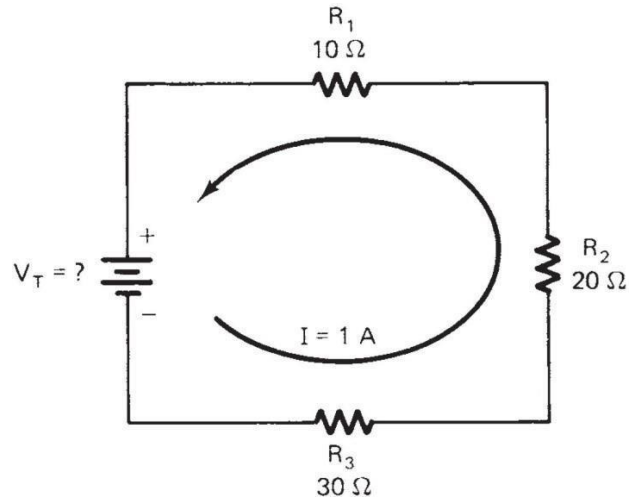
14. Find the equivalent resistance of the given circuit.



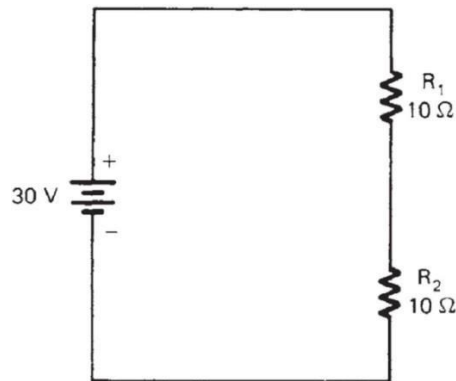
15. Find the value of  $V_T$  in the given circuit.  
 16. Find the voltage across each resistance in the given circuit.



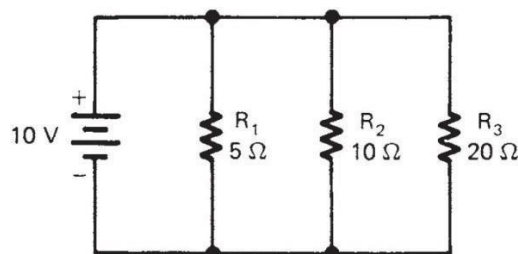
17. A potential difference of 4V is applied to two resistors of  $6\ \Omega$  and  $2\ \Omega$  connected in series. Calculate: (a) the combined resistance (b) the current flowing (c) the potential difference across the  $6\ \Omega$  resistor  
 18. Resistors of  $20\ \Omega$ ,  $20\ \Omega$  and  $30\ \Omega$  are connected in parallel. What resistance must be added in series with the combination to obtain a total resistance of  $10\ \Omega$ .  
 19. If four identical lamps are connected in parallel and the combined resistance is  $100\ \Omega$ , find the resistance of one lamp.  
 20. Find the current across the each resistance and total current flowing in the given circuit.



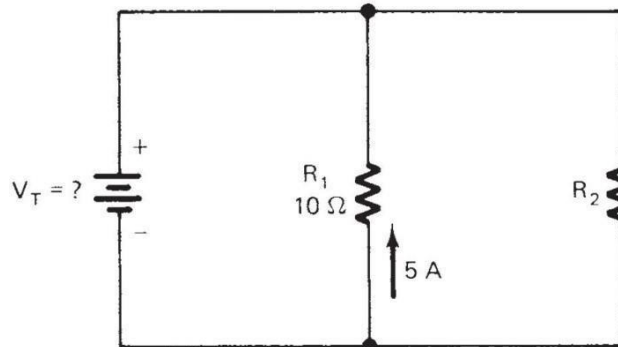
21. In the given circuit, the resistance  $R_1$  and  $R_2$  are connected in parallel. (i) Find the value of  $V_T$ . (ii) Find the total current and equivalent resistance in the circuit if resistance  $R_2 = 10\Omega$



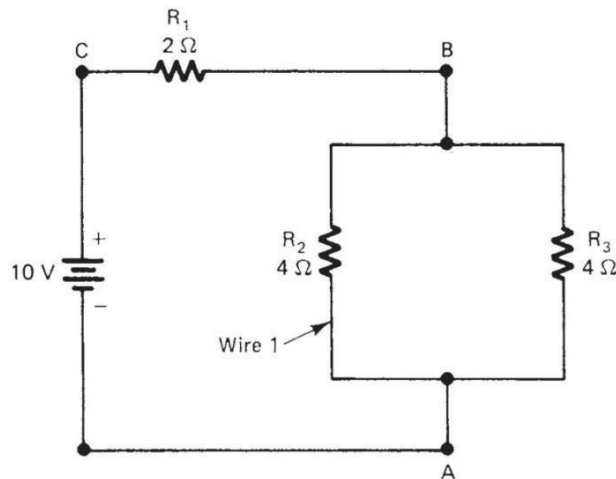
22. In the given circuit, (i) find the equivalent resistance of the circuit and total current flowing in the circuit. (ii) find the current flowing through  $R_2$  and  $R_3$ . (iii) find the voltage across each resistance.



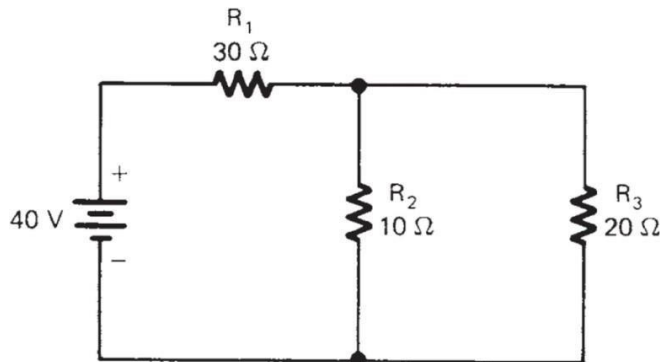
23. In the given circuit, (i) find the equivalent resistance and total current flowing in the circuit. (ii) find the voltage and current across each resistance in the circuit.



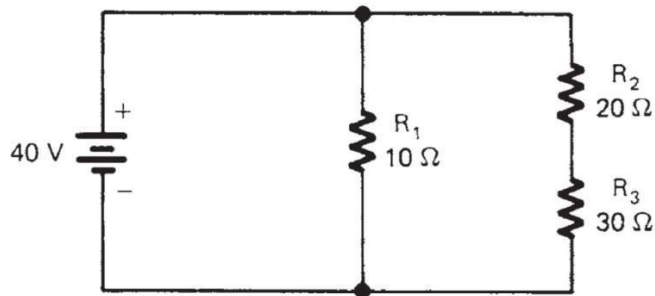
24. In the given circuit, (i) find the equivalent resistance and total current flowing in the circuit. (ii) find the voltage and current across each resistance in the circuit.







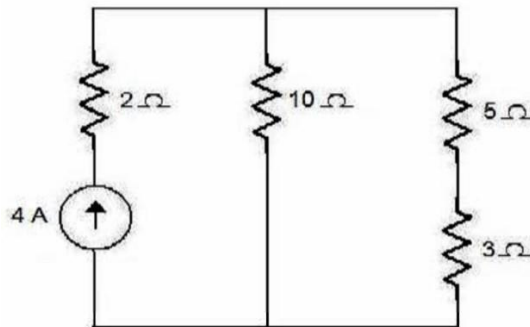
25. Find the current through 10 ohm resistor for the following circuit.



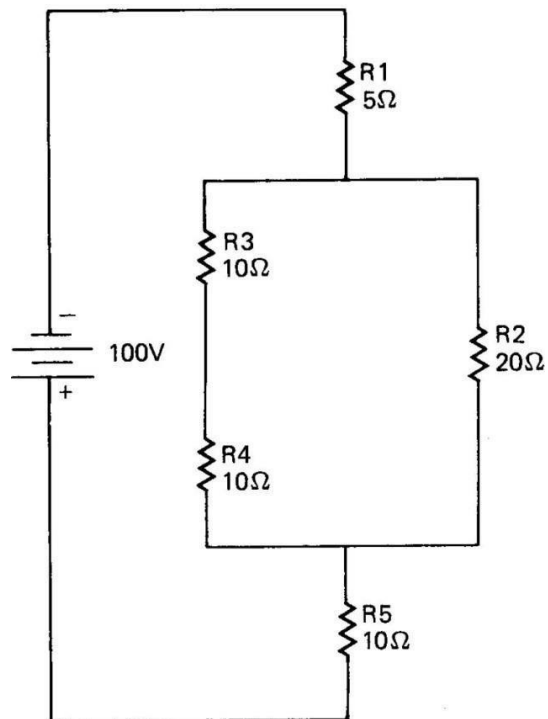
26. In the given circuit, (i) find the equivalent resistance and total current flowing in the circuit. (ii) find the voltage and current across each resistance in the circuit.



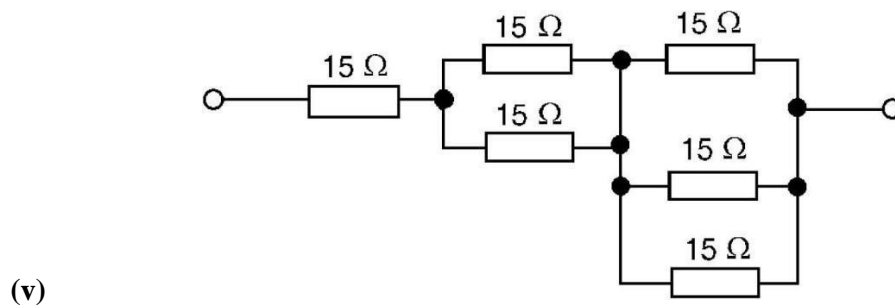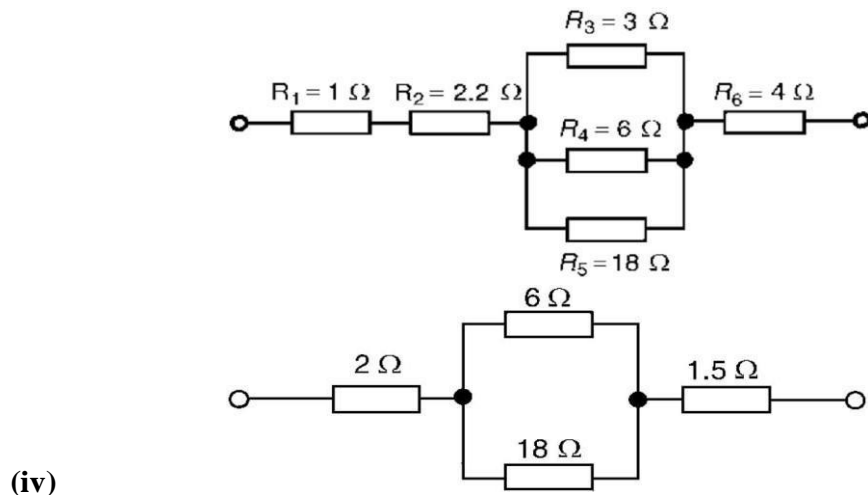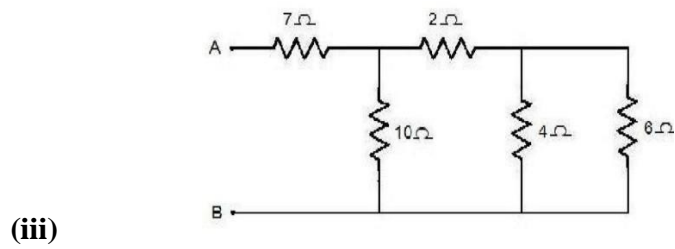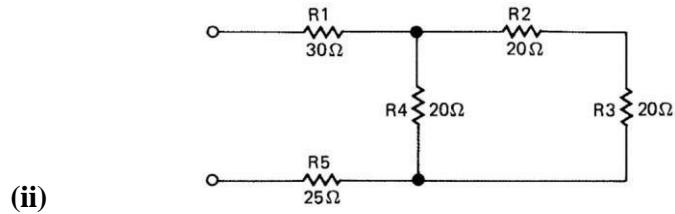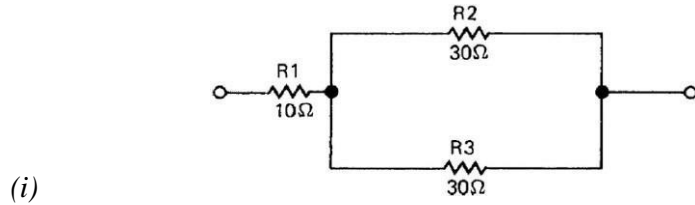
27. Find the equivalent resistance of the following circuits:



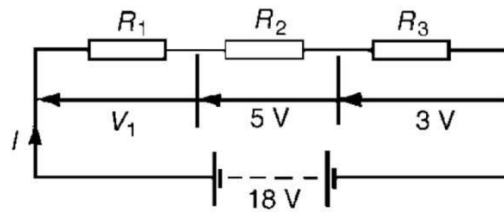
28. For the circuit shown in below Figure, determine the value of  $V_1$ . If the total circuit resistance is  $36\Omega$ , determine the supply current and the value of resistors  $R_1$ ,  $R_2$  and  $R_3$ .



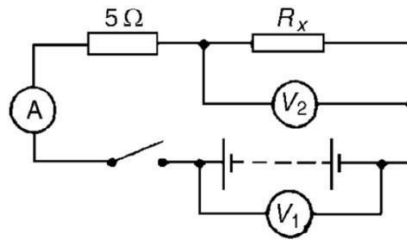29. When the switch in the circuit in below Figure is closed the reading on voltmeter 1 is 30 V and that on voltmeter 2 is 10 V. Determine the reading on the ammeter and the value of resistor  $R_x$ .




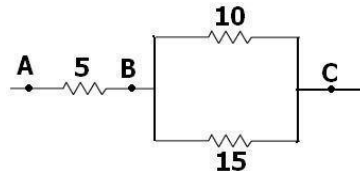30. A potential difference of 6V is applied to two resistors of  $3\Omega$  and  $6\Omega$  connected in parallel. Calculate:  
 (a) the combined resistance (b) the current flowing in the main circuit (c) the current flowing in the  $3\Omega$  resistor.
31. Three resistors are connected as shown in the diagram:




Through the resistor  $5\Omega$  ohm, a current of 1A is flowing.

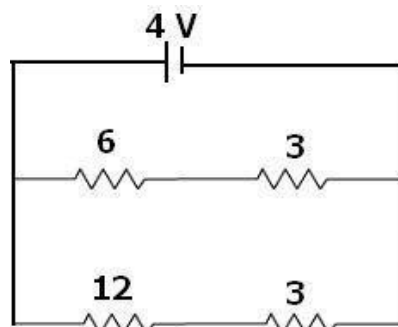- What is the current through the other two resistors?
  - What is the p.d. across AB and across AC?
  - What is the total resistance?
32. For the circuit shown in the diagram below:




What is the value of: (i) current through  $6\Omega$  resistor? (ii) p.d. across  $12\Omega$  resistor?

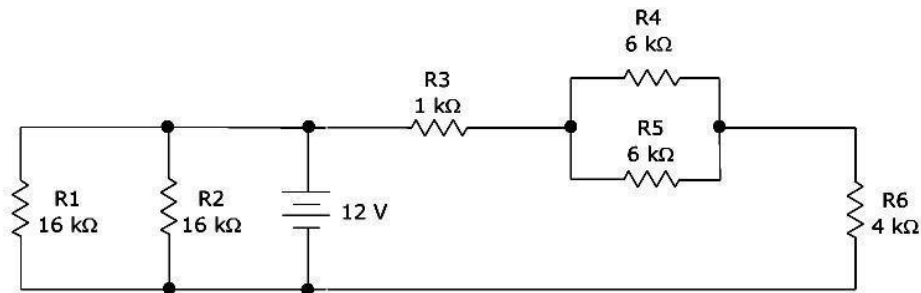
33. Calculate the total resistance of the circuit below, as seen by the voltage source.



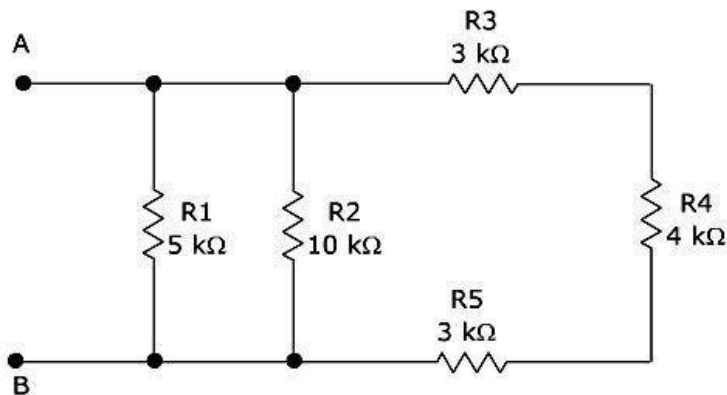34. What is the resistance between A and B in the given figure given below?



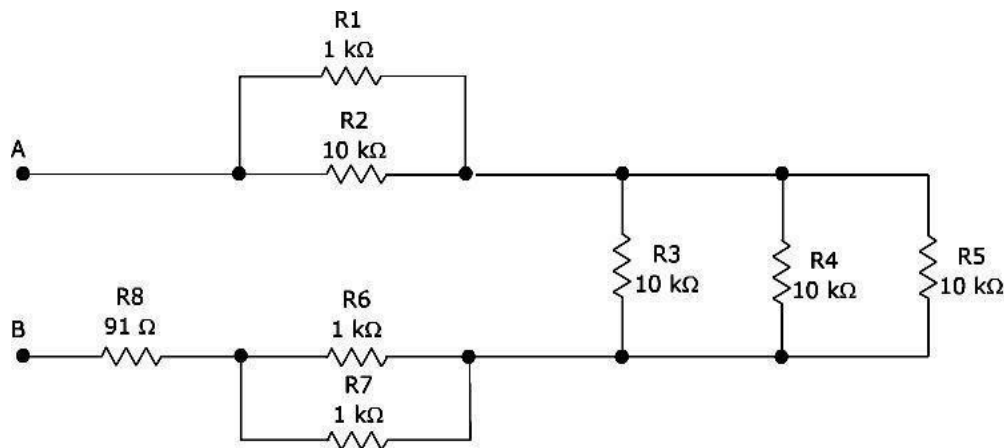
35. What is the resistance between A and B in the given figure given below?



36. Resistances of  $4\Omega$  and  $12\Omega$  are connected in parallel across a 9 V battery. Determine (a) the equivalent circuit resistance, (b) the supply current, and (c) the current in each resistor.
37. Three identical lamps A, B and C are connected in series across a 150 V supply. State (a) the voltage across each lamp, and (b) the effect of lamp C failing.
38. The p.d's measured across three resistors connected in series are 5 V, 7 V and 10 V, and the supply current is 2 A. Determine (a) the supply voltage, (b) the total circuit resistance and (c) the values of the three resistors.
39. If three identical lamps are connected in parallel and the combined resistance is  $150\Omega$ , find the resistance of one lamp.

### NUMERICAL PROBLEMS

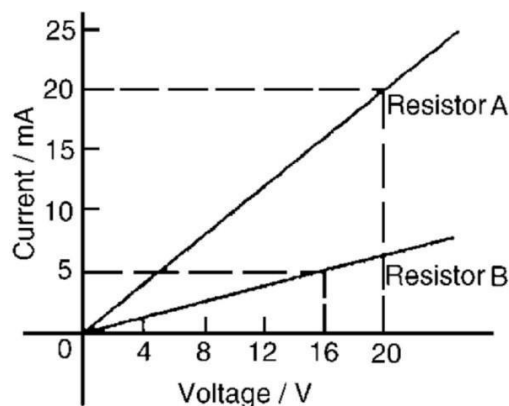1. What will be the current drawn by an electric bulb of 40 W when it is connected to a source of 220V?
2. A bulb is rated as 250V;0.4A. Find its power and resistance.
3. An electric bulb is connected to a 220V power supply line. If the bulb draw a current of 0.5A, calculate the power of the bulb.
4. An electric bulb is connected to a 250 V generator. The current is 0.50 A. What is the power of the bulb?
5. What current will be taken by a 920W appliance if the supply voltage is 230V?
6. When an electric lamp is connected to 12V battery, it draws a current 0.5A. Find the power of the lamp.
7. Calculate the power used in  $2\Omega$  resistor in each (i) a 6V battery in series with  $1\Omega$  and  $2\Omega$  resistor (ii) a 4V battery in parallel with  $12\Omega$  and  $2\Omega$ resistor.
8. A 100 W electric light bulb is connected to a 250 V supply. Determine (a) the current flowing in the bulb, and (b) the resistance of the bulb.
9. Calculate the power dissipated when a current of 4 mA flows through a resistance of  $5k\Omega$
10. An electric kettle has a resistance of  $30\Omega$ . What current will flow when it is connected to a 240 V supply? Find also the power rating of thekettle.
11. A current of 5 A flows in the winding of an electric motor, the resistance of the winding being  $100\Omega$ . Determine (a) the p.d. across the winding, and (b) the power dissipated by the coil.
12. The current/voltage relationship for two resistors A and B is as shown in below Figure. Determine the value of the resistance of each resistor and also find the power dissipated through each resistor.



13. The hot resistance of a 240 V filament lamp is  $960\Omega$ . Find the current taken by the lamp and its power rating.
14. A 12 V battery is connected across a load having a resistance of  $40\Omega$ . Determine the current flowing in the load, the power consumed and the energy dissipated in 2 minutes.
15. A source of e.m.f. of 15 V supplies a current of 2 A for six minutes. How much energy is provided in this time?
16. Electrical equipment in an office takes a current of 13 A from a 240 V supply. Estimate the cost per week of electricity if the equipment is used for 30 hours each week and 1 kWh of energy costs 7p
17. An electric heater consumes 3.6 MJ when connected to a 250 V supply for 40 minutes. Find the power rating of the heater and the current taken from the supply.
18. Determine the power dissipated by the element of an electric fire of resistance  $20\Omega$  when a current of 10 A flows through it. If the fire is on for 6 hours determine the energy used and the cost if 1 unit of electricity costs 7p.
19. A business uses two 3 kW fires for an average of 20 hours each per week, and six 150 W lights for 30 hours each per week. If the cost of electricity is 7p per unit, determine the weekly cost of electricity to the business.
20. If 5 A, 10 A and 13 A fuses are available, state which is most appropriate for the following appliances which are both connected to a 240 V supply (a) Electric toaster having a power rating of 1 kW (b) Electric fire having a power rating of 3 kW
21. The hot resistance of a 250 V filament lamp is  $625\Omega$ . Determine the current taken by the lamp and its power rating.
22. Determine the resistance of a coil connected to a 150 V supply when a current of  
(a) 75 mA (b) 300 mA flows through it. Determine the power dissipated through it.
23. Determine the resistance of an electric fire which takes a current of 12 A from a 240 V supply. Find also the power rating of the fire and the energy used in 20 h.
24. Determine the power dissipated when a current of 10 mA flows through an appliance having a resistance of 8 k.
25. 85.5 J of energy are converted into heat in nine seconds. What power is dissipated?
26. A current of 4 A flows through a conductor and 10 W is dissipated. What p.d. exists across the ends of the conductor?
27. Find the power dissipated when:  
(a) a current of 5 mA flows through a resistance of 20 k  
(b) a voltage of 400 V is applied across a 120 k resistor  
(c) a voltage applied to a resistor is 10 kV and the current flow is 4 mA.



28. A battery of e.m.f. 15 V supplies a current of 2 A for 5 min. How much energy is supplied in this time?
29. In a household during a particular week three 2 kW fires are used on average 25 h each and eight 100 W light bulbs are used on average 35 h each. Determine the cost of electricity for the week if 1 unit of electricity costs 7p.
30. Calculate the power dissipated by the element of an electric fire of resistance 30  $\Omega$  when a current of 10 A flows in it. If the fire is on for 30 hours in a week determine the energy used. Determine also the weekly cost of energy if electricity costs 7.2p per unit.
31. A television set having a power rating of 120 W and electric lawnmower of power rating 1 kW are both connected to a 240 V supply. If 3 A, 5 A and 10 A fuses are available state which is the most appropriate for each appliance.
32. For a heater rated at 4kW and 220V, calculate: (a) the current (b) the resistance of the heater (c) the energy consumed in 2 hours and (d) the cost if 1kWh is priced at Rs.4.60
33. A radio set of 60W runs for 50hrs. How much electrical energy consumed?
34. A current of 4A flows through a 12V car headlight bulb for 10min. How much energy transfer occurs during this time?
35. Calculate the energy transferred by a 5A current flowing through a resistor of 2 $\Omega$  for 30min.
36. A bulb is rated at 200V-100W. What is its resistance? 5 such bulbs burn for 4 hrs. What is the electrical energy consumed? Calculate the cost if the rate is Rs. 4.60 per unit.
37. A refrigerator having a power rating of 350W operates for 10 hours a day. Calculate the cost of electrical energy to operate it for a month of 30 days. The rate of electrical energy is Rs. 3.40 per kWh.
38. What will be the current drawn by an electric bulb of 40W when it is connected to a source of 220V?
39. An electric bulb is rated 220V and 100W. When it is operated on 110V, find the power consumed.
40. An electric heater draws a current of 10A from a 220V supply. What is the cost of using the heater for 5 hrs every day for 30 days if the cost of 1 unit is Rs.5.20?
41. In house two 60W electric bulbs are lighted for 4 hrs and three 100W bulbs for 5 hrs every day. Calculate the electrical energy consumed in 30 days.
42. An electric motor takes 5A current from a 220V supply line. Calculate the power of the motor and electrical energy consumed by it in 2hrs.
43. An electric iron consumes energy at a rate of 840 W when heating is at the maximum rate and 360W when the heating is at the minimum. The voltage is 220V. What are the current and the resistance in each case?
44. An electric refrigerator rated 400 W operates 8 hour/day. What is the cost of the energy to operate it for 30 days at Rs 3.00 per kWh?

45. An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h.
46. Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220V?
47. Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?
48. Two bulbs A and B are rated 100W – 120V and 10W – 120V respectively. They are connected across a 120V source in series. Which will consume more energy.
49. Two bulbs A and B are rated 100W – 120V and 10W – 120V respectively. They are connected across a 120V source in series. Find the current in each bulb. Which will consume more energy.
50. An electric kettle is rated at 230V, 1000W. What is the resistance of its element? What maximum current can pass through its element?
51. An electric geyser has the rating 1000W, 220V marked on it. What should be the minimum rating in whole number of a fuse wire that may be required for safe use with this geyser?
52. The mains power supply of a house is through a 5A fuse. How many 100W, 220V bulbs can be used in this house at the correct voltage?
53. An electrician puts a fuse of rating 5A in that part of domestic electrical circuit in which an electrical heater of rating 1.5kW, 220V is operating. What is likely to happen in this case and why? What change if any needs to be made?
54. Two bulbs of ratings 40W-220V and 60W-220V are connected in series and this combination is connected with a supply of 220V. Calculate the current from the supply line.
55. Two bulbs have the ratings 40W-200V and 20W-110V. What is the ratio of their resistances?
56. I can spend Rs. 9 per month (30 days) on electric light. If power is 30 paise per kWh and I use 5 identical bulbs for 5 hours a day, what should be the power of each bulb?
57. Compute the number of electrons passing through per minute through an electric bulb of 60W, 220V.
58. If electrical energy costs Rs. 3 per unit, what is the total cost of leaving 4 light bulbs rated at 100W each switched on for 8 hours.
59. An electric heater of resistance  $8\Omega$  draws 15 A from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.
60. 100 J of heat are produced each second in a  $4\Omega$  resistance. Find the potential difference across the resistor.
61. Compute the heat generated while transferring 96000 coulomb of charge in one hour through a potential difference of 50V.

62. An electric iron of resistance  $20\ \Omega$  takes a current of  $5\ \text{A}$ . Calculate the heat developed in  $30\ \text{s}$ .
63. A p.d. of  $250\ \text{V}$  is applied across a resistance of  $500\ \Omega$  in an electric iron. Calculate (i) current (ii) heat energy produced in joules in  $10\ \text{s}$ .
64. Calculate the heat produced when  $96000\ \text{C}$  of charge is transferred in  $1\ \text{hour}$  through a p.d. of  $50\ \text{V}$ .
65. A resistance of  $40\ \Omega$  and one of  $60\ \Omega$  are arranged in series across  $220\ \text{V}$  supply. Find the heat in joules produced by this combination of resistances in half a minute?
66. When a current of  $4\ \text{A}$  passes through a certain resistor for  $10\ \text{min}$ ,  $2.88 \times 10^4\ \text{J}$  of heat are produced. Calculate (a) power of the resistor (b) the voltage across the resistor.
67. A heating coil has a resistance of  $200\ \Omega$ . At what rate will heat be produced in it when a current of  $2.5\ \text{A}$  flows through it.
68. An electric heater of resistance  $8\ \Omega$  takes a current of  $15\ \text{A}$  from the mains supply line. Calculate the rate at which heat is developed in the heater.
69. A resistance of  $25\ \Omega$  is connected to a  $12\ \text{V}$  battery. Calculate the heat energy in joule generated per minute.
70. How much heat will an instrument of  $12\ \text{W}$  produce in one minute if it is connected to a battery of  $12\ \text{V}$ ?

### **GIST OF THE LESSON**

1. **Positive and negative charges:** The charge acquired by a glass rod when rubbed with silk is called positive charge and the charge acquired by an ebonite rod when rubbed with wool is called negative charge.
2. **Coulomb:** It is the S.I. unit of charge. One coulomb is defined as that amount of charge which repels an equal and similar charge with a force of  $9 \times 10^9\ \text{N}$  when placed in vacuum at a distance of  $1\ \text{meter}$  from it. Charge on an electron =  $-1.6 \times 10^{-19}\ \text{coulomb}$ .
3. **Static and current electricities:** Static electricity deals with the electric charges at rest while the current electricity deals with the electric charges in motion.
4. **Conductor:** A substance which allows passage of electric charges through it easily is called a conductor. A conductor offers very low resistance to the flow of current. For example copper, silver, aluminium etc.
5. **Insulator:** A substance that has infinitely high resistance does not allow electric current to flow through it. It is called an insulator. For example rubber, glass, plastic, ebonite etc.
6. **Electric current:** The flow of electric charges across a cross-section of a conductor constitutes an electric current. It is defined as the rate of flow of the electric charge through any section of a conductor.

$$\text{Electric current} = \text{Charge/Time or}$$

$$I = Q/t$$

Electric current is a scalar quantity.

7. **Ampere:** It is the S.I. unit of current. If one coulomb of charge flows through any section of a conductor in one second, then current through it is said to be one ampere.  
 $1 \text{ ampere} = 1 \text{ coulomb} / 1 \text{ second}$  or  
 $1 \text{ A} = 1 \text{ C} / 1 \text{ s} = 1 \text{ C s}^{-1}$  1 milliampere = 1 mA =  $10^{-3} \text{ A}$   
1 microampere =  $1 \mu\text{A} = 10^{-6} \text{ A}$
8. **Electric circuit:** The closed path along which electric current flows is called an electric circuit.
9. **Conventional current:** Conventionally, the direction of motion of positive charges is taken as the direction of current. The direction of conventional current is opposite to that of the negatively charged electrons.
10. **Electric field:** It is the region around a charged body within which its influence can be experienced.
11. **Electrostatic potential:** Electrostatic potential at any point in an electric field is defined as the amount of work done in bringing a unit positive charge from infinity to that point. Its unit is volt. Positive charges move from higher to lower potential regions. Electrons, being negatively charged, move from lower to higher potential regions.
12. **Potential difference between two points:** The Potential difference between two points in an electric field is the amount of work done in bringing a unit positive charge from one to another. Potential difference = Work done/Charge or  $V = W/Q$
13. **One volt potential difference:** The Potential difference between two points in an electric field is said to be one volt if one joule of work has to be done in bringing a positive charge of one coulomb from one point to another.  $1 \text{ volt} = 1 \text{ joule} / 1 \text{ coulomb}$  or  $1 \text{ V} = 1 \text{ J} / 1 \text{ C}$
14. **Galvanometer:** It is a device to detect current in an electric circuit.
15. **Ammeter:** It is a device to measure current in a circuit. It is always connected in series in a circuit.
16. **Voltmeter:** It is a device to measure potential difference. It is always connected in parallel to the component across which the potential difference is to be measured.
17. **Ohm's law:** This law states that the current passing through a conductor is directly proportional to the potential difference across its ends, provided the physical conditions like temperature, density etc. remain unchanged.

$$V \propto I \text{ or } V = RI$$

The proportionality constant R is called resistance of conductor.

18. **Resistance:** It is a property of a conductor by virtue of which it opposes the flow of current through it.

It is equal to the ratio of the potential difference applied across its ends and the current flowing through it.

Resistance = Potential difference/Current

$$\text{or } R = V/I$$

- 19. Ohm:** It is the S.I. unit of resistance. A conductor has a resistance of one ohm if a current of one ampere flows through it on applying a potential difference of one volt across its ends.

$$1 \text{ ohm} = 1 \text{ volt/1 ampere} \quad \text{or} \quad 1\Omega = 1\text{V}/1\text{A}$$

- 20. Factors on which resistance of a conductor depends:** The resistance  $R$  of a conductor depends

- i) Directly on its length  $L$  i.e.  $R \propto L$ .
- ii) inversely on its area of cross-section  $A$  i.e.  $R \propto 1/A$
- iii) on the nature of material of the conductor on. On combining the above factors, we get  
 $R \propto L/A$

$R = \rho * L/A$  The proportionality constant  $\rho$  is called resistivity of conductor.

- 21. Resistivity:** It is defined as the resistance offered by a cube of a material of side 1 m when current flows perpendicular to its opposite faces. Its S.I. unit is ohm-meter ( $\Omega\text{m}$ ). Resistivity,  $\rho = RA/L$

- 22. Equivalent resistance:** If a single resistance can replace the combination of resistances in such a manner that the current in the circuit remains unchanged, then that single resistance is called the equivalent resistance.

**23. Laws of resistances in series:**

- i) Current through each resistance is same.
- ii) Total voltage across the combination = Sum of the voltage drops.  
 $V = V_1 + V_2 + V_3$
- iii) Voltage drops across any resistor is proportional to its resistance.  
 $V_1 = IR_1, V_2 = IR_2, V_3 = IR_3$
- iv) Equivalent resistance = Sum of the individual resistances.  
 $R_s = R_1 + R_2 + R_3$
- v) Equivalent resistance is larger than the largest individual resistance.

**24. Laws of resistances in parallel:**

- i) Voltage across each resistance is same and is equal to the applied voltage.
- ii) Total current = Sum of the currents through the individual resistances.  
 $I = I_1 + I_2 + I_3$
- iii) Currents through various resistances are inversely proportional to the individual resistances.

$$I_1 = V/R_1, I_2 = V/R_2, I_3 = V/R_3$$

- iv) Reciprocal of equivalent resistance = Sum of reciprocals of individual resistances.  $1/R_p = 1/R_1 + 1/R_2 + 1/R_3$
- v) Equivalent resistance is less than the smallest individual resistance.

- 25. Joule's law of heating:** It states that the heat produced in a conductor is directly proportional to (i) the square of the current  $I$  through it (ii) proportional to its resistance  $R$  and (iii) the time  $t$  for which current is passed. Mathematically, it can be expressed as  $H = I^2 R t$  joule =  $I^2 R t / 4.18 \text{ cal}$

or

$$H = V I t \quad \text{joule} = V I t / 4.18 \text{ cal}$$

- 26. Electric energy:** It is the total work done in maintaining an electric current in an electric circuit for given time.

$$\text{Electric energy, } W = V I t = I^2 R t \text{ joule}$$

- 27. Electrical power:** Electrical power is the rate at which electric energy is consumed by an appliance.

$$P = W/t = V I = I^2 R = V^2/R$$

- 28. Watt:** It is the S.I. unit of power. The power of an appliance is 1 watt if one ampere of current flows through it on applying a potential difference of 1 volt across it.

$$1 \text{ watt} = 1 \text{ joule} / 1 \text{ second} = 1 \text{ volt} \times 1 \text{ ampere}$$

$$\text{or } 1 \text{ W} = 1 \text{ Js}^{-1} = 1 \text{ VA}$$

$$1 \text{ kilowatt} = 1000 \text{ W}$$

- 29. Kilowatt hour:** It is the commercial unit of electrical energy. One kilowatt hour is the electric energy consumed by an appliance of 1000 watts when used for one hour.

$$1 \text{ kilowatt hour (kWh)} = 3.6 \times 10^6 \text{ J}$$

\*\*\*